

Bioinstrumentation

© Springer Nature Switzerland AG 2022

Reprint of original edition © Morgan & Claypool 2006

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means—electronic, mechanical, photocopy, recording, or any other except for brief quotations in printed reviews, without the prior permission of the publisher.

Bioinstrumentation

John D. Enderle

ISBN: 978-3-031-00488-9 paperback

ISBN: 978-3-031-01616-5 ebook

DOI 10.1007/978-3-031-01616-5

Library of Congress Cataloging-in-Publication Data

A Publication in the Springer series

SYNTHESIS LECTURES ON BIOMEDICAL ENGINEERING

Lecture #6

Series Editor and Affiliation: John D. Enderle, University of Connecticut

1930-0328 Print

1930-0336 Electronic

First Edition

10 9 8 7 6 5 4 3 2 1

Portions of this manuscript were reprinted from the following book with the Permission of Elsevier, *INTRODUCTION TO BIOMEDICAL ENGINEERING*, ISBN 0122386626 2005, Chapter 8, pp403–504, Enderle et al 2nd edition. This permission is granted for non-exclusive world English rights only in both print and on the world wide web.

Additional Information regarding the bestselling book, *Introduction to Biomedical Engineering*, 2nd edition 2005, by Enderle, Blanchard and Bronzino, from Elsevier can be found on the Elsevier Homepage <http://www.elsevier.com>.

Bioinstrumentation

John D. Enderle

Program Director & Professor for Biomedical Engineering
University of Connecticut

SYNTHESIS LECTURES ON BIOMEDICAL ENGINEERING #6

ABSTRACT

This short book provides basic information about bioinstrumentation and electric circuit theory. Many biomedical instruments use a transducer or sensor to convert a signal created by the body into an electric signal. Our goal here is to develop expertise in electric circuit theory applied to bioinstrumentation. We begin with a description of variables used in circuit theory, charge, current, voltage, power and energy. Next, Kirchhoff's current and voltage laws are introduced, followed by resistance, simplifications of resistive circuits and voltage and current calculations. Circuit analysis techniques are then presented, followed by inductance and capacitance, and solutions of circuits using the differential equation method. Finally, the operational amplifier and time varying signals are introduced. This lecture is written for a student or researcher or engineer who has completed the first two years of an engineering program (i.e., 3 semesters of calculus and differential equations). A considerable effort has been made to develop the theory in a logical manner—developing special mathematical skills as needed. At the end of the short book is a wide selection of problems, ranging from simple to complex.

KEYWORDS

Bioinstrumentation, Circuit Theory, Introductory Biomedical Engineering, Sensors, Transducers, Circuits, Voltage, Current

Contents

1.	Introduction	1
2.	Basic Bioinstrumentation System	5
3.	Charge, Current, Voltage, Power and Energy	7
3.1	Charge	7
3.2	Current	7
3.2.1	Kirchhoff's Current Law	9
3.3	Voltage	11
3.3.1	Kirchhoff's Voltage Law	12
3.4	Power and Energy	13
3.5	Sources	14
4.	Resistance	17
4.1	Resistors	17
4.2	Power	19
4.3	Equivalent Resistance	22
4.4	Series and Parallel Combinations of Resistance	23
4.4.1	Resistors in Series	23
4.4.2	Resistors in Parallel	24
4.5	Voltage and Current Divider Rules	26
4.5.1	Voltage Divider Rule	26
4.5.2	Current Divider Rule	27
5.	Linear Network Analysis	31
5.1	Node-Voltage Method	31
5.2	Mesh-Current Method	39
5.3	Linearity, Superposition and Source Transformations	44
5.3.1	Linearity and Superposition	44
5.3.2	Equivalent Sources	48
6.	Thévenin's and Norton's Theorems	53
6.1	Thévenin's Theorem	53
6.2	Norton's Theorem	56

6.3	Dependent Sources and Thévenin and Norton Equivalent Circuits	59
7.	Inductors	63
7.1	Power and Energy	67
8.	Capacitors	71
8.1	Power and Energy	76
9.	Inductance and Capacitance Combinations	79
10.	General Approach to Solving Circuits Involving Resistors, Capacitors and Inductors	89
10.1	Discontinuities and Initial Conditions in a Circuit	96
10.2	Circuits with Switches	111
11.	Operational Amplifiers	119
11.1	Voltage Characteristics of the Op Amp	130
12.	Time-Varying Signals	133
12.1	Phasors	134
12.2	Passive Circuit Elements in the Phasor Domain	135
12.3	Kirchhoff's Laws and Other Techniques in the Phasor Domain	137
13.	Active Analog Filters	141
14.	Bioinstrumentation Design	153
14.1	Noise	153
14.2	Computers	154
13.	Exercises	157

Preface

This short book on bioinstrumentation is written for a reader who has completed the first two years of an engineering program (i.e., three semesters of calculus and differential equations). A considerable effort has been made to develop the theory in a logical manner—developing special mathematical skills as needed.

I have found it best to introduce this material using simple examples followed by more difficult ones.

At the end of the short book is a wide selection of problems, ranging from simple to difficult, presented in the same general order as covered in the textbook.

I acknowledge and thank William Pruehsner for the technical illustrations. Portions of this short book are from Chapter 8 of Enderle, J. D., Blanchard, S. M., and Bronzino, J. D., *Introduction to Biomedical Engineering (Second Edition)*, Elsevier, Amsterdam, 2005, 1118 pages, with Sections 1, 2 and 13 contributed by Susan Blanchard, Amanda Marley, and H. Troy Nagle.